

# EE3331C: Modeling Electrical Circuits

Arthur Tay

ECE, NUS

## Physical laws

1. Two basic laws:

- conservation of charge: Kirchhoff's current law
- conservation of energy: Kirchhoff's voltage law

2. Voltage-current relationship:

- Resistor:  $v(t) = Ri(t)$
- Capacitor:  $v_c(t) = \frac{1}{C} \int i(\tau) d\tau$   
the capacitance  $C$  of a capacitor is a measure of how much charge can be stored for a given voltage difference across the element, with units of charge per volt (i.e. farad (F)).
- Inductor:  $v_L(t) = L \frac{di(t)}{dt}$   
the unit of inductance  $L$  is the henry (H) which is one volt-second per ampere.

The resistor, capacitor and inductor voltage-current relationships together with the conservation of charge and conservation of energy can be used to obtain circuit models.

## Circuit analysis with impedances

1. Impedance:

- idea: resistance resists/'impedes' current flow:  $\frac{v}{i} = R$
- capacitance and inductance elements also impede the flow of current
- impedance is defined as the ratio of a voltage transform  $V(s)$  to a current transform  $I(s)$ , i.e.  $Z(s) = \frac{V(s)}{I(s)}$  (or the transfer function from current,  $I(s)$  to voltage,  $V(s)$ ).
- note that in time domain,  $v$  and  $i$  are related by convolution, i.e.  $v = z * i$ .
- impedance of resistor is thus:  $Z_R(s) = R$ .

- impedance of capacitor:

$$v(t) = \frac{1}{C} \int_0^t i(\tau) d\tau$$

LT gives  $V(s) = \frac{1}{Cs} I(s)$  with zero initial voltage

$$\Rightarrow Z(s) = \frac{V(s)}{I(s)} = \frac{1}{Cs}$$

- impedance of inductor:

$$v(t) = L \frac{di(t)}{dt}$$

LT gives  $V(s) = Ls I(s)$  with zero initial current

$$\Rightarrow Z(s) = \frac{V(s)}{I(s)} = Ls$$

## 2. Series and parallel impedances:

- concept of impedance useful, individual elements can be combined in series or parallel law;
- key assumption, initial conditions for inductor and capacitor are zero;
- two or more impedances are in series if they have the *same current*, the total impedance is the sum of the individual impedance:

$$Z(s) = Z_1(s) + \dots + Z_n(s)$$

e.g. the series RLC circuit, the equivalent impedance is given by

$$Z(s) = R + sL + \frac{1}{sC} = \frac{LCs^2 + RCs + 1}{sC}$$


- two or more impedances are in parallel if they have the *same voltage difference* across them, their impedances combine by the reciprocal rule:

$$\frac{1}{Z(s)} = \frac{1}{Z_1(s)} + \dots + \frac{1}{Z_n(s)}$$


e.g. the parallel RLC circuit, the equivalent total impedance is

$$\frac{1}{Z(s)} = \frac{1}{R} + \frac{1}{sL} + \frac{1}{1/(Cs)} = \frac{RLCs^2 + Ls + R}{RLs}$$

$$Z(s) = \frac{RLs}{RLCs^2 + Ls + R}$$

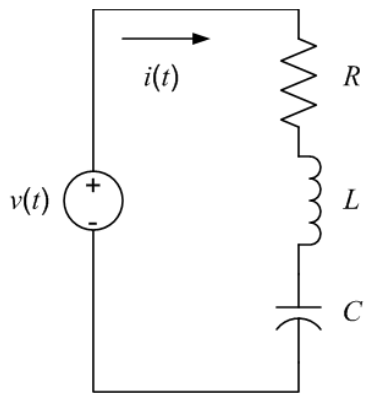


(a) Series RLC circuit

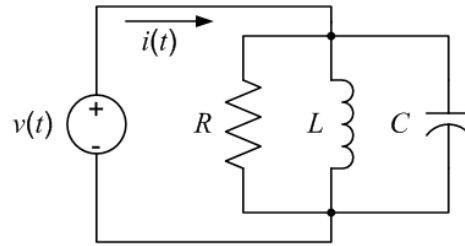

(b) Parallel RLC circuit

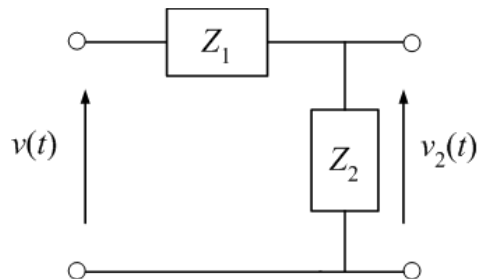
3. Voltage divider rule:

$$V_2(s) = \frac{Z_2(s)}{Z_1(s) + Z_2(s)} V(s)$$



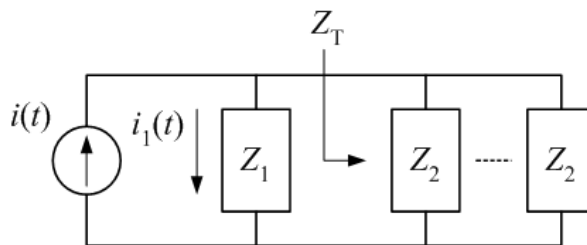4. Current divider rule:

$$I_1(s) = \frac{Z_T(s)}{Z_1(s) + Z_T(s)} I(s)$$



## Practice Problems

1. Consider the following circuit:

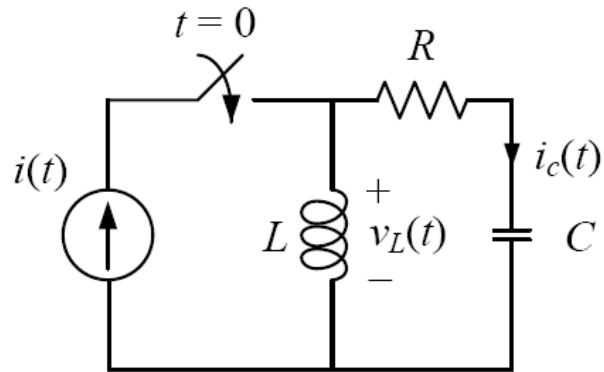


Figure 1: Q1

- (i) Find the transfer function relating the input current,  $i(t)$ , to capacitor current,  $i_c(t)$ .
  - (ii) Find the transfer function relating the input current,  $i(t)$ , to the inductor voltage,  $v_L(t)$ .
2. Consider the following parallel RLC circuit:

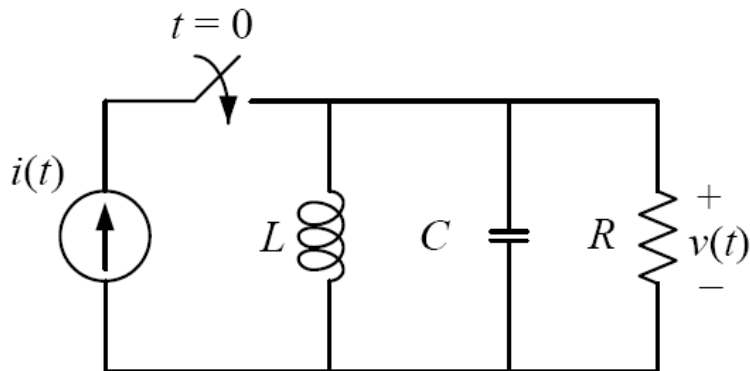


Figure 2: Q2

- (i) Find the differential equation that relates the input current,  $i(t)$ , to the voltage,  $v(t)$ .
- (ii) Find the transfer function,  $G(s) = \frac{V(s)}{I(s)}$ .

3. Consider the following series RLC circuit:

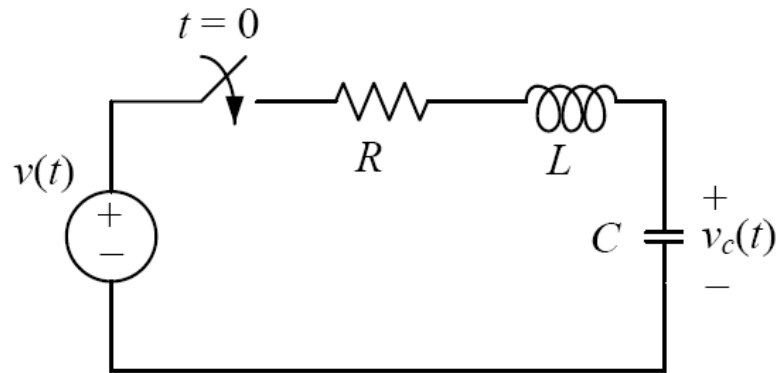


Figure 3: Q3

- (i) Find the differential equation relating the source voltage,  $v(t)$ , to capacitor voltage,  $v_c(t)$ .
- (ii) Find the transfer function,  $G(s) = \frac{V_c(s)}{V(s)}$ .
- (iii) Given  $R = 4\omega$ ,  $L = 1\text{H}$  and  $C = 0.24\text{F}$ , find  $v_c(t)$  when  $v(t) = U(t)$ .

4. Consider the following circuit:

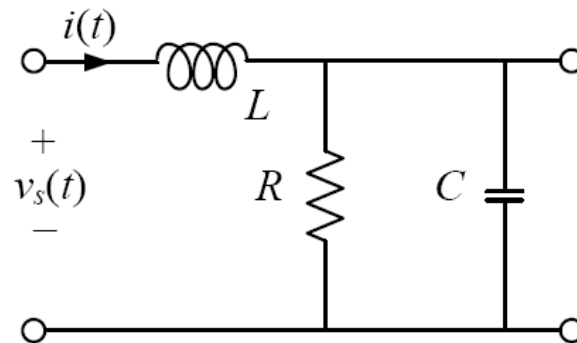


Figure 4: Q4

- (i) Find the differential equation relating the source voltage,  $v(t)$ , to the current,  $i(t)$ .
- (ii) Find the transfer function,  $G(s) = \frac{I(s)}{V(s)}$ .

5. Consider the following coupled RC circuit:

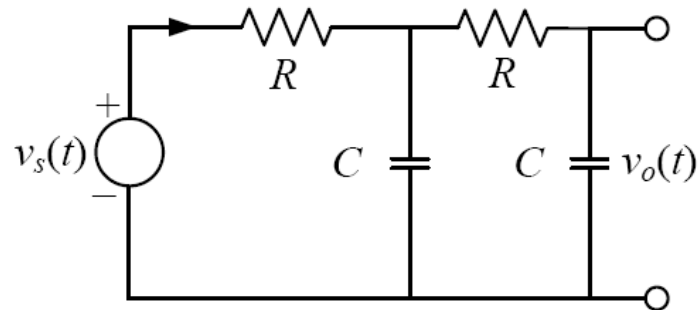


Figure 5: Q5

(i) Find the transfer function,  $G(s) = \frac{V_o(s)}{V_s(s)}$ .

6. Consider the following electrical circuit:

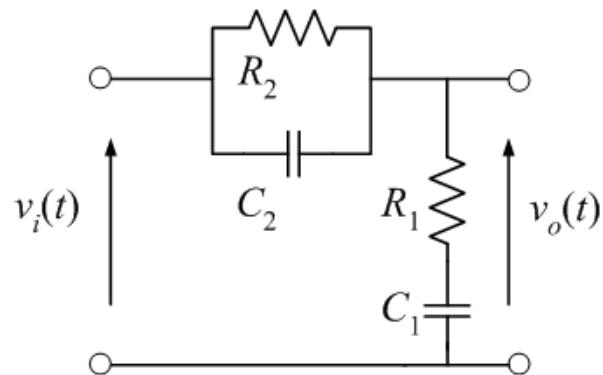


Figure 6: Q6

(i) Find the transfer function,  $G(s) = \frac{V_o(s)}{V_i(s)}$ .